



## Chapter 4 – Practical Circuits

Rectifier Circuits

Batteries and Chargers

Connectors



**ARRL** *The national association for  
AMATEUR RADIO*

# Power Supplies

Power supplies provide the necessary power, voltage and current requirements for electronic devices.

- 13.8 V supplies for transceivers
- High Voltage supplies for amplifiers.
- Alternate power



# Power Supply Parts


- Transformer – steps AC voltage up or down.
- Rectifier Diodes – change AC to pulsating DC.
- Filter Network – includes capacitors and inductors to smooth out the pulses.
- Voltage Regulator – keeps the voltage constant.
- Protection –
  - Crowbar circuit for Overvoltage.
  - Voltage Foldback circuit for Overcurrent.



**ARRL** The national association for  
AMATEUR RADIO



# Rectifiers – Half Wave and Full Wave

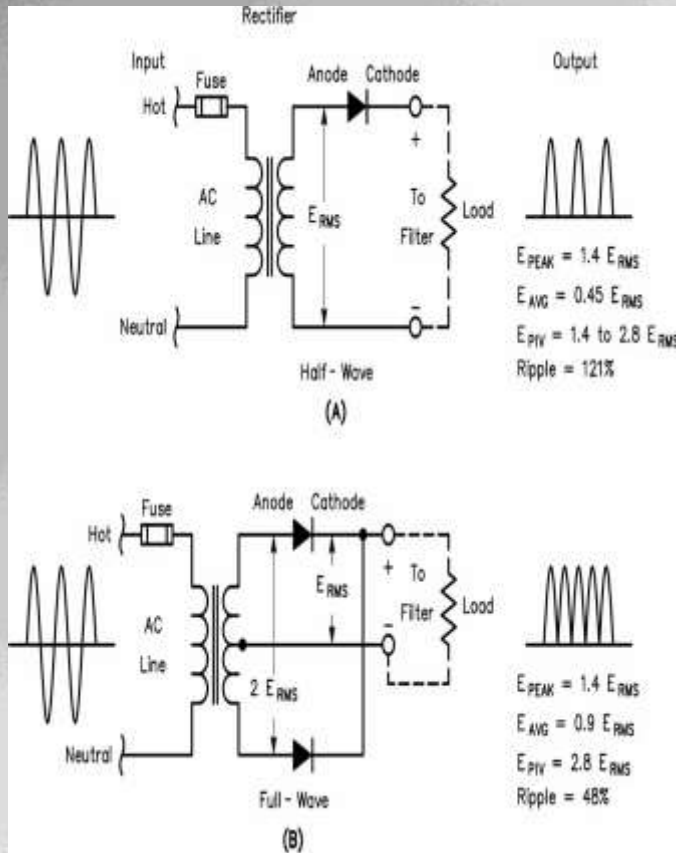


- Diodes conduct only when anode is positive.
- Diode in Half Wave conducts for one half cycle –  $180^\circ$
- Diodes in Full Wave each conduct on alternate half cycles –  $360^\circ$
- Full Wave ripple frequency is twice the line frequency.
- Peak voltage across the diodes when not conducting is  $2 * E_{PK} = 2.828 * E_{RMS}$



**ARRL** The national association for AMATEUR RADIO



# Rectifiers – Full Wave Bridge

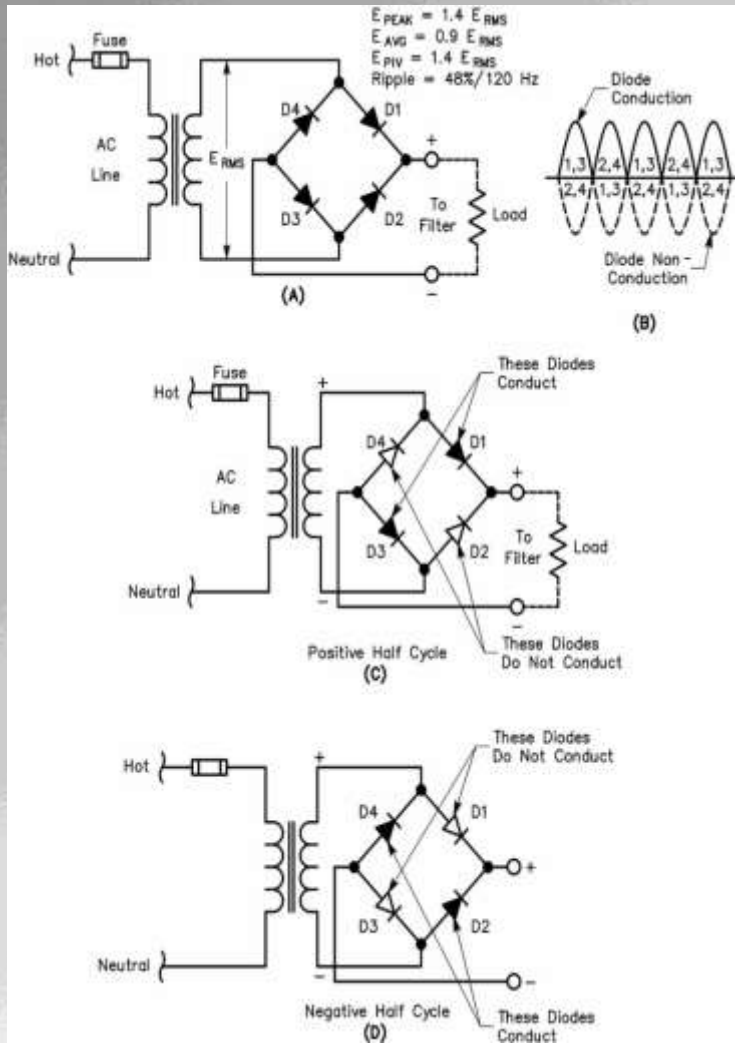

- Two diodes conduct on each half cycle.
- Output ripple frequency is twice the line frequency.
- Peak voltage across the diodes when not conducting is  $E_{PK} = 1.414 * E_{RMS}$
- Compared to Full Wave for same voltage to Load:
  - Transformer secondary voltage is half as large.
  - Transformer secondary current is twice as large.
  - Diode Peak Inverse Voltage is half as large.
  - Load voltage is lower by one extra diode drop,  $\sim 1.4V$  vs.  $0.5V$



**ARRL** The national association for AMATEUR RADIO



# Rectifier Ratings

## *Peak Inverse Voltage – PIV*

- Voltage across the diode when not conducting
- $2 \times E_{\text{peak}}$  minimum for half-wave and full-wave
- $1 \times E_{\text{peak}}$  minimum for bridge.
- Increase voltage capacity by adding additional diodes with parallel equalizing resistors.

## *Average Forward Current*

- Current through the diode when conducting. Highest in half-wave for the same power out.
- Increase current capacity by adding additional diodes with series equalizing resistors in parallel.



**ARRL** The national association for  
AMATEUR RADIO



# Power Supply Filtering

The ripple must be smoothed out to make DC.

- Ripple is removed with a filter network of
  - Large capacitors – capacitor input filter
  - Inductors and Capacitors – Choke input filter
- Capacitor charges to peak when diode conducts and discharges until next diode conducts.
- Voltage variation depends on load and size of capacitor.
- *Regulation* is the percent change from no-load to full-load.



**ARRL** The national association for  
AMATEUR RADIO



# Power Supply Filter Capacitors

*Electrolytic* capacitors are best for low voltage power supply filters – high capacitance in small volume compared to oil and paper.

- The AC current from charging and discharging causes losses in the capacitor due to the *Equivalent Series Resistance – ESR*.
- Capacitor voltage rating should be larger than the peak inverse voltage.
- Hum and noise on signals is often caused by open or failed filter capacitors.



**ARRL** The national association for  
AMATEUR RADIO





# Power Supply Safety

Grounding means connecting the metal case of the PS to the Electrical Ground. Connections must be made with UL approved connectors.

- Neutral and ground are connected together at one point. (By National Electric Code: **Only at the main load center.**)
- Ground Fault Circuit Interrupters: GFCI
- A switch and fuse should be provided to disconnect the AC power.



# High Voltage Power Supply Safety

A dangerous supply can be anything over 30 Volts or containing more than 5 Joules.

- Filter capacitors hold a charge a long time, and may be charged to the output voltage of the power supply.
- After turning off power, check the high voltage with a meter or discharge the high voltage with a shorting probe before working on the supply.
- Bleeder resistors across the filter capacitors “bleed off” charge when supply is turned off




**ARRL** The national association for  
AMATEUR RADIO


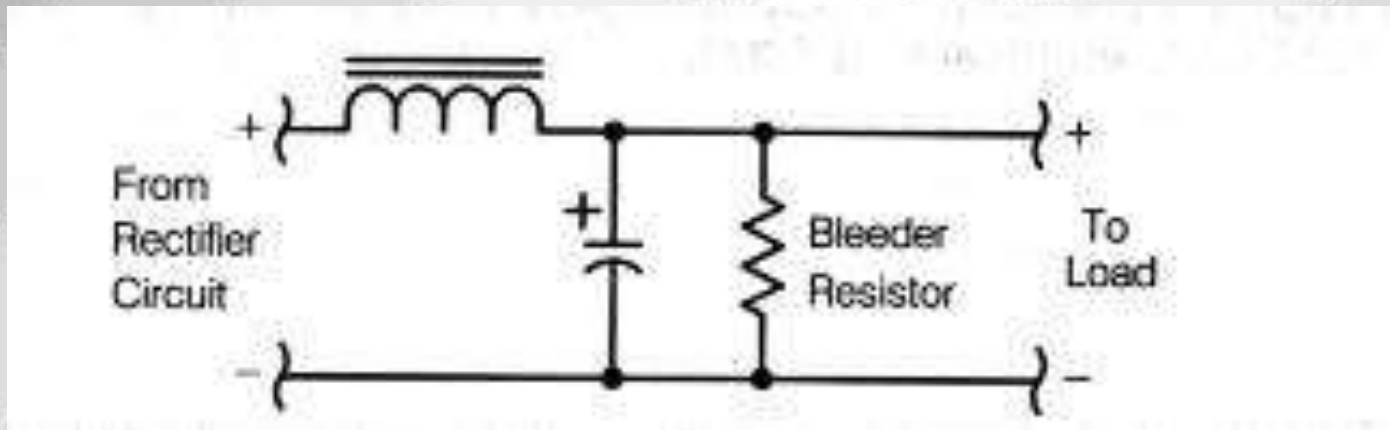
# Bleeder Resistors

A bleeder resistor is installed across the filter capacitors as a safety feature to make sure that the capacitors are discharged.



**ARRL** The national association for  
AMATEUR RADIO



# Switching Power Supplies

Switchmode power supplies can be small and lightweight and very efficient. Almost all modern powers supplies, including those in PCs, are switching power supplies.


- Some disadvantages are complexity and RF interference.
- Because they operate at high frequencies, the transformers and capacitors can be smaller.
- Capacitors must have low ESR and also low Equivalent Series Inductance, ESL.



**ARRL** The national association for  
AMATEUR RADIO



# Switching Power Supplies

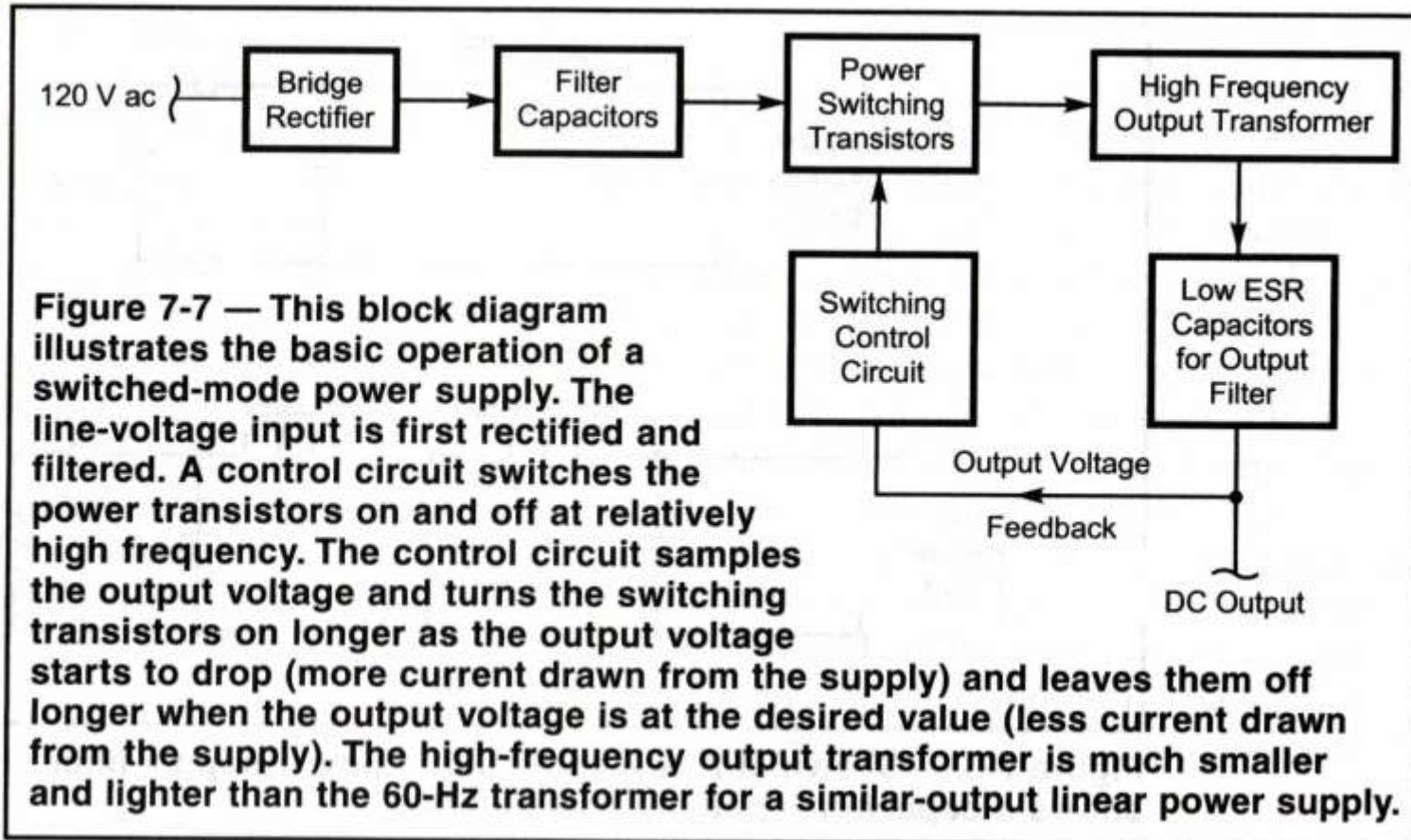

**ARRL** The national association for  
AMATEUR RADIO



# Batteries

Two basic types:

- *Primary* or Non-rechargeable.
- *Secondary* or Rechargeable.
- Rechargeable battery types based on battery chemistry
  - NiCd, NiMH – Low internal resistance, high discharge
  - Li-Ion – Large energy density makes for small size
  - Lead Acid – *Storage Batteries*
    - 2.3 Volts per cell
    - 13.6 Volt battery useful down to 10.5 Volts
    - Over-discharging will reduce battery life.



# Battery Charging

Batteries should be charged at the rate and method recommended by the manufacturer.

- Use a charger designed for the type of battery.
- NEVER attempt to charge primary batteries such as carbon-zinc, alkaline, or silver-nickel.
- Lead-Acid storage batteries may generate hydrogen gas while charging. Do it in a well ventilated area.



# Alternative Power Sources for Off-Grid

Solar power is *Photovoltaic Conversion* using large PN junction cells.

- Photons give electrons energy to cross the PN
- Current from the cell makes an open-circuit voltage of 0.5Volts.
- Cells are connected in series-parallel
- Efficiency is about 20% but sunlight can be up to 1000 watts per square meter.

A storage battery is necessary for night time.

- A series diode keeps the cell from discharging the battery.




**ARRL** The national association for  
AMATEUR RADIO





# AC Power Connectors

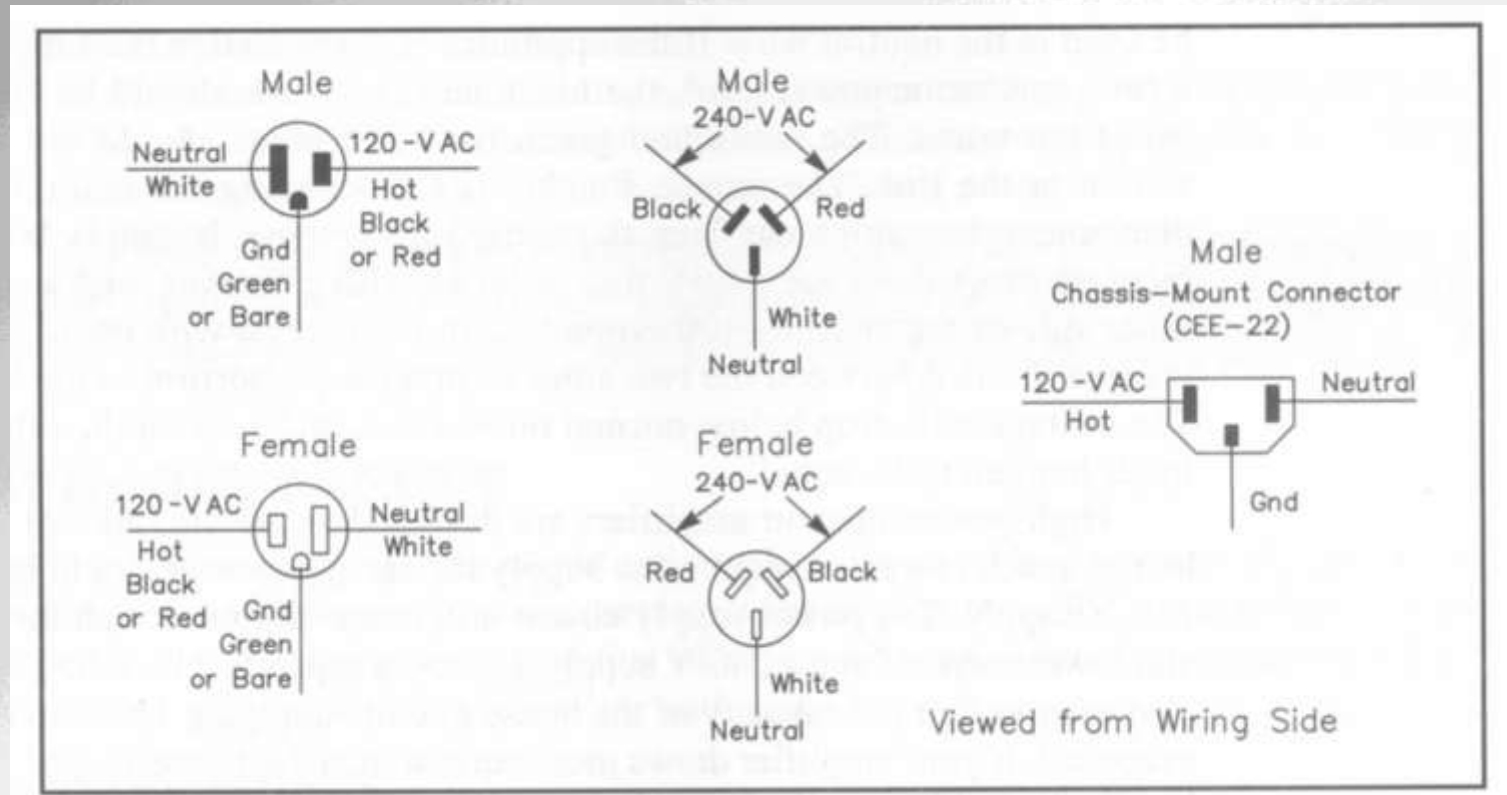

**ARRL** The national association for  
AMATEUR RADIO



# DC Power Connectors

- Molex – White nylon multi-conductor
- Coaxial – Common on “wall warts”
- PowerPoles – Sexless single conductor units can be combined into multi-conductor
- Binding Posts – for terminals or bare wires
- Automotive crimped terminals
- Terminals should be crimped with proper tool.
- Don't use solder for high current without a crimped or mechanical connection.



**ARRL** The national association for  
AMATEUR RADIO



# Signal Connectors

Connectors for audio and control signals need reliable contact at low currents.

- Plugs are on cables, Jacks are on equipment.
- Mating connectors should have an index key.
- Placing similar connectors close together can result in mixed up connections.
- RCA Phono plugs and jacks
- DIN and Mini-DIN multi-conductor
- Microphones: 8-Pin Round; RJ-45



**ARRL** The national association for  
AMATEUR RADIO



# RF Connectors

RF connectors can cause losses and reflections at higher frequencies. The connector must be rated for the voltage, current, and frequency.

- Common types: UHF, N, C, BNC, SMA
- UHF connector – PL259, SO239 – is OK For HF (and VHF) at amateur power levels.
- For UHF, type N is useable to 10GHz.
- Connectors used outside must be waterproof or sealed.



# Data Connectors

Several connector families commonly used in computing equipment and newer amateur equipment.

- D-Type – commonly called DB-25, DB-9, etc. P or S suffix denotes Pins or Sockets, i.e., DB-9P, used for PC COM serial ports.
- USB – Becoming common for radio ↔ computer.
- USB ↔ RS232 adapters
- Ethernet RJ-45



**ARRL** The national association for  
AMATEUR RADIO





**ARRL** *The national association for*  
**AMATEUR RADIO**

